

Final Project

David Rohweder

CMPEN 331

May 7, 2022

Abstract

In the final project for CMPEN 331 we sought to implement a forwarding functionality to the existing CPU schema. The reason to modify the circuit was to prevent data hazards from occurring which prevents data coherence. To achieve this functionality two multiplexers are added to the circuit to choose what input source new instructions should pull data from if the control unit detects a potential hazard will occur for the given instruction operands.

Introduction

When designing this implementation of a CPU there are five distinct processing regions in which the instructions are executed. To begin, on each cycle a instruction from the instruction memory unit will read the instruction at the pc count then increment to the next $pc + 4$. Next, after the instruction is fetched it will be decoded in the instruction decode unit where the opcode, function, rs, rt, rd, and imm value will be read. After, the control unit will process the opcode to determine what instruction type it is (R-type or I-type). From this information the control unit will determine if the instruction is writing to the memory, writing from the memory to the register, or writing to the register. Furthermore, the control unit will determine the alu operation to perform on the rs and rt registers and if an I-type word to use the aluimm value. A new feature is forwarding and if the control unit detects a data hazard in rs or rt it will determine where to pull the most recent data from. The output of the control unit feeds into 3 multiplexors to determine if an I-type to use rt as the destination register, if a hazard is in rs to use which source of data, and if a hazard is in rt to use which source of data. Next, the data is passed to the exe phase where the ALU determines whether to use the aluimm or rt value in processing. After, the ALU performs the computation based on the ALU code determined by the control unit. The output of the exe phase is then sent to the memory phase where if the control unit determines we save the result of the ALU to the data memory or not. Next, the data is passed from the data memory phase to the write back phase, where either the data memory result or the ALU computation result is stored in the register, and then if the control unit wants that result to be saved to the register then that data is placed into either the determined rd or rt register place.

These commands are executed in a pipeline fashion where instructions are being computed together, each at a different phase of the phases described above (IF, ID, EXE, MEM, and WB) and as seen in *Figure 1*.

The benefit of an architecture as shown in *Figure 1* is a pipelined, data hazard free CPU which can process instructions much faster than if run serially and a data coherent system where the data will always be reflected correctly.

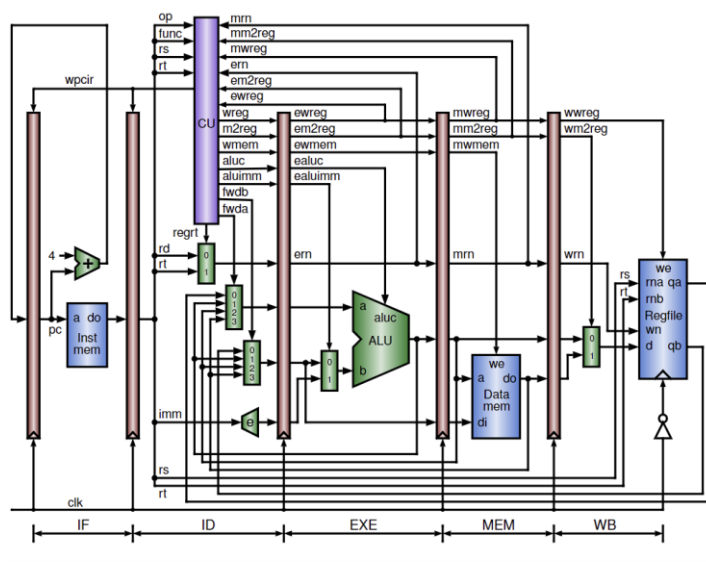


Figure 1: Circuit Schema

Verilog Design Code:

Device: XC7Z010CLG400-1

Test bench code:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: PSU CMPEN 331
// Engineer: David Rohweder
//
// Create Date: 03/21/2022 04:25:25 PM
// Design Name:
// Module Name: testbench
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module testbench();
    reg clock;
    wire [31:0]pc;
    wire [31:0]dinstOut;
    wire ewreg;
    wire em2reg;
    wire ewmem;
    wire [3:0]ealuc;
    wire ealuimm;
    wire [4:0]ern;
    wire [31:0]eqa;
    wire [31:0]eqb;
```

```

wire [31:0]eimm32;

wire mwreg;

wire mm2reg;

wire mwmem;

wire [4:0]mrn;

wire [31:0]mr;

wire [31:0]mqb;

wire wwreg;

wire [4:0]wrn;

wire wm2reg;

wire [31:0]wr;

wire [31:0]wdo;

wire [31:0]r; // project

wire [31:0]mdo; // project

```

```

initial begin

    clock = 0;

end

```

```

datapath dataP(clock, pc, dinstOut, ewreg, em2reg, ewmem, ealuc, ealuimm, ern, eqa, eqb, eimm32, mwreg, mm2reg, mwmem, mrn, mr, mqb, wwreg, wrn,
wm2reg, wr, wdo, r, mdo);

```

```

always begin

    #5

    clock = ~clock;

end

```

```

endmodule

```

Datapath code:

```

`timescale 1ns / 1ps

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

// University: Penn State

// Engineer: David Rohweder

//

// Create Date: 03/21/2022 06:08:38 PM

// Design Name: 331 final project

// Module Name: datapath

// Project Name:

// Target Devices:

// Tool Versions:

// Description:

```

```
//  
// Dependencies:  
//  
// Revision:  
// Revision 0.01 - File Created  
// Additional Comments:  
//  
////////////////////////////////////
```

```
module datapath(  
    input clock,  
    output wire [31:0]pc,  
    output wire [31:0]dinstOut,  
    output wire ewreg,  
    output wire em2reg,  
    output wire ewmem,  
    output wire [3:0]ealuc,  
    output wire ealuimm,  
    output wire [4:0]ern, // project  
    output wire [31:0]eqa,  
    output wire [31:0]eqb,  
    output wire [31:0]eimm32,  
    output wire mwreg,  
    output wire mm2reg,  
    output wire mwmem,  
    output wire [4:0]mrn, // project  
    output wire [31:0]mr,  
    output wire [31:0]mqb,  
    output wire wwreg,  
    output wire [4:0]wrn, // project  
    output wire wm2reg,  
    output wire [31:0]wr,  
    output wire [31:0]wdo,  
    output wire [31:0]r, // project  
    output wire [31:0]mdo // project  
);
```

```
wire [31:0]nextPc;  
wire [31:0]instOut;
```

```

programCounter pcc(nextPc, clock, pc);
pcAddr pcA(pc, nextPc);
instructionMemory instMem(pc, instOut);
ifid_pipelineRegister ifidRP(instOut, clock, dinstOut);

wire [5:0]opcode = dinstOut[31:26];
wire [5:0]func = dinstOut[5:0];
wire [4:0]rt = dinstOut[20:16];
wire [4:0]rd = dinstOut[15:11];
wire [4:0]rs = dinstOut[25:21];

wire wreg;
wire m2reg;
wire wmem;
wire [3:0]aluc;
wire aluimm;
wire regrt;
wire [1:0]fwdb; // project
wire [1:0]fwda; // project
controlUnit contUnit(opcode, func, rs, rd, rt, mrn, mm2reg, mwreg, ern, em2reg, ewreg, wreg, m2reg, wmem, aluc, aluimm, regrt, fwdb, fwda);

wire [31:0]wbData;
wire [4:0]destReg;
wire [31:0]qa;
wire [31:0]qb;
muxRegrt muxR(rt, rd, regrt, destReg);
regFile regF(rs, rt, wrn, wbData, wwreg, ~clock, qa, qb);

wire [31:0]fqa;
wire [31:0]fqb;
muxForwardA fdmxa(fwda, qa, r, mr, mdo, fqa);
muxForwardB fdmxb(fwdb, qb, r, mr, mdo, fqb);

wire [15:0]imm = dinstOut[15:0];
wire [31:0]imm32;
immediateExtender immediateExt(imm, imm32);
idexe_pipelineRegister idexeRP(wreg, m2reg, wmem, aluc, aluimm, destReg, fqa, fqb, imm32, clock, ewreg, em2reg, ewmem, ealuc, ealuimm, ern, eqa, eqb, eimm32);

wire [31:0]b;

```

```

aluMux i_aluMux(eqb, eimm32, ealuimm, b);

alu i_alu(eqa, b, ealuc, r);

exeMem i_exeMem(ewreg, em2reg, ewmem, ern, r, eqb, clock, mwreg, mm2reg, mwmem, mrn, mr, mqb);

dataMemory i_dataMemory(mr, mqb, mwmem, clock, mdo);

memWB i_memWB(mwreg, mm2reg, mrn, mr, mdo, clock, wwreg, wm2reg, wrn, wr, wdo);


wbData wbMux(wr, wdo, wm2reg, wbData);

```

```

endmodule

```

```

// *****
// Region Project
// *****

```

```

module muxForwardA(
    input [1:0]fwda,
    input [31:0]qa,
    input [31:0]r,
    input [31:0]mr,
    input [31:0]mdo,
    output reg [31:0]fqa
);

```

```

always @(*) begin

```

```

    case (fwda)
        2'b00: begin
            fqa = qa;
        end

```

```

        2'b01: begin
            fqa = r;
        end

```

```

        2'b10: begin
            fqa = mr;
        end

```



```
        2'b11: begin
            fqa = mdo;
        end

    endcase
end

endmodule
```

```
module muxForwardB(
    input [1:0]fwdb,
    input [31:0]qb,
    input [31:0]r,
    input [31:0]mr,
    input [31:0]mdo,
    output reg [31:0]fqb
);
```

```
always @(*) begin
```

```
    case (fwdb)
        2'b00: begin
            fqb = qb;
        end
```

```
        2'b01: begin
            fqb = r;
        end
```

```
        2'b10: begin
            fqb = mr;
        end
```

```
        2'b11: begin
            fqb = mdo;
        end
```

```
    endcase
```

```
end
```

```
endmodule
```

```
// *****  
// End Region Project  
// *****
```

```
// *****  
// Region Lab 5  
// *****
```

```
module wbData(  
    input [31:0]wr,  
    input [31:0]wdo,  
    input wm2reg,  
    output reg [31:0]wbData  
);
```

```
always @(*) begin  
    if (wm2reg == 0) begin  
        wbData = wr;  
    end else if (wm2reg == 1) begin  
        wbData = wdo;  
    end  
end  
end
```

```
endmodule
```

```
// *****  
// Region Lab 4  
// *****
```

```
module aluMux(  
    input [31:0]eqb,
```

```
input [31:0]eimm32,
```

```
input ealuimm,
```

```
output reg [31:0]b
```

```
);
```

```
always @(*) begin
```

```
    if (ealuimm == 0) begin
```

```
        b = eqb;
```

```
    end else if (ealuimm == 1) begin
```

```
        b = eimm32;
```

```
    end
```

```
end
```

```
endmodule
```

```
module alu(
```

```
    input [31:0]eqa,
```

```
    input [31:0]b,
```

```
    input [3:0]ealuc,
```

```
    output reg [31:0]r
```

```
);
```

```
always @(*) begin
```

```
    case (ealuc)
```

```
        4'b0010: begin
```

```
            r = eqa + b; // add
```

```
        end
```

```
        4'b0110: begin
```

```
            r = eqa - b; // sub
```

```
        end
```

```
        4'b0001: begin
```

```
            r = eqa | b; // or
```

```
        end
```

```
        4'b1001: begin
```

```
            r = eqa ^ b; // xor
```

end

4'b0000: begin

r = eqa & b; // and

end

endcase

end

endmodule

module exeMem(

input ewreg,

input em2reg,

input ewmem,

input [4:0]ern,

input [31:0]r,

input [31:0]eqb,

input clock,

output reg mwreg,

output reg mm2reg,

output reg mwmem,

output reg [4:0]mrn,

output reg [31:0]mr,

output reg [31:0]mqb

);

always @(posedge clock) begin

mwreg = ewreg;

mm2reg = em2reg;

mwmem = ewmem;

mrn = ern;

mr = r;

mqb = eqb;

end

endmodule

```

module dataMemory(
    input [31:0]mr,
    input [31:0]mqb,
    input mwmem,
    input clock,
    output reg [31:0]mdo
);
reg [31:0] memory[0:63];

initial begin
    memory[0] = 32'h00000000;
    memory[1] = 32'hA00000AA;
    memory[2] = 32'h10000011;
    memory[3] = 32'h20000022;
    memory[4] = 32'h30000033;
    memory[5] = 32'h40000044;
    memory[6] = 32'h50000055;
    memory[7] = 32'h60000066;
    memory[8] = 32'h70000077;
    memory[9] = 32'h80000088;
    memory[10] = 32'h90000099;
end

always @(*) begin
    mdo = memory[mr[7:2]];
end

always @(negedge clock) begin
    if (mwmem == 1) begin
        memory[mr] = mqb;
    end
end

endmodule

```

```

module memWB(
    input mwreg,
    input mm2reg,
    input [4:0]mrn,

```

```
input [31:0]mr,
input [31:0]mdo,
input clock,
output reg wwreg,
output reg wm2reg,
output reg [4:0]wrn,
output reg [31:0]wr,
output reg [31:0]wdo
);
```

```
always @(posedge clock) begin
    wwreg = mwreg;
    wm2reg = mm2reg;
    wrn = mrn;
    wr = mr;
    wdo = mdo;
end
```

```
endmodule
```

```
// *****
// End Region Lab 4
// *****
```

```
// *****
// Region Lab 3
// *****
```

```
module programCounter (
    input [31:0]nextPc,
    input clock,
    output reg [31:0]pc
);
```

```
initial begin
    pc <= 100;
end
```

```

// at pos edge of clock pc = nextPc

always @(posedge clock) begin

    pc = nextPc;

end

endmodule


// memory implemented as 2D reg arr, on any signal change instOut is set to value of meory array at pc pos
// implementation - 256 bytes or 64 words (4b / word): byte addr dif from word addr: pc = 100 == word addr 25
// only need to init memory where instrurt is located -- words 25 and 26 ++ any signal change
module instructionMemory (

    input [31:0]pc,

    output reg [31:0]instOut

);

    reg [31:0] memory[0:63];

    initial begin // format 6-bit opcode, 5-bit rs, 5-bit rt, 5-bit rd, 5-bit offset, 6-bit unused

        memory[25] = {6'b000000, 5'b00001, 5'b00010, 5'b00011, 5'b00000, 6'b100000}; // add $3, %1, $2
        memory[26] = {6'b000000, 5'b01001, 5'b00011, 5'b00100, 5'b00000, 6'b100010}; // sub $4, %9, $3
        memory[27] = {6'b000000, 5'b00011, 5'b01001, 5'b00101, 5'b00000, 6'b100101}; // or $5, %3, $9
        memory[28] = {6'b000000, 5'b00011, 5'b01001, 5'b00110, 5'b00000, 6'b100110}; // xor $6, %3, $9
        memory[29] = {6'b000000, 5'b00011, 5'b01001, 5'b00111, 5'b00000, 6'b100100}; // and $7, %3, $9

    end

    always @(*)begin

        instOut = memory[pc[7:2]];

    end

endmodule


// on any signal change
module pcAddr (

    input [31:0]pc,

    output reg [31:0]nextPc

);

    reg [31:0]hardwired;

```

[illegible]


```
output reg [3:0]aluc, // 4 bits - op we intend to exe on ALu
```

```
output reg aluimm, // alu immediate when 1, indicates we want to use sign extended im over qb in ALU, if we want qb aluimm = 0
```

```
output reg regrt, // reg rt - when 1 indicates we are writing to rt not rd in regfile. if rd regrt = 0. regrt -> dont care val if wreg = 0
```

```
output reg [1:0]fwdb,
```

```
output reg [1:0]fwda
```

```
);
```

```
always @(*)begin
```

```
    if (mm2reg == 1 || mwreg == 1 || em2reg == 1 || ewreg == 1) begin // does hazard potentially exist || if em2reg = 1 then we stall bc we have not read  
mdo yet
```

```
        if (ern == rs || ern == rt || mrn == rs || mrn == rt) begin // does any of the registers have a hazard
```

```
            ///
```

```
            if (ern == rs || ern == rt) begin
```

```
                if (ern == rs) begin
```

```
                    fwda = 2'b01; // load qa = r
```

```
                    fwdb = 2'b00; // load qb = qb
```

```
                end
```

```
            if (ern == rt) begin
```

```
                fwda = 2'b00; // load qa = qa
```

```
                fwdb = 2'b01; // load qb = r
```

```
            end
```

```
        end
```

```
        ///
```

```
        ///
```

```
        if (mrn == rs || mrn == rt) begin
```

```
            if (mrn == rs) begin
```

```
                fwda = 2'b10; // load qa = mr
```

```
                fwdb = 2'b00; // load qb = qb
```

```

end

if (mrn == rt) begin

    fwda = 2'b00; // load qa = qa
    fwdb = 2'b10; // load qb = mr

end

end

///

// chefs note: since there is a not clock on reg file that on neg edge trigger values are read so if a write happens on pos then no hazzard occurs..

end
end else begin

    fwda = 2'b00; // load qa = qa
    fwdb = 2'b00; // load qa = qb
end

case (opcode)
    6'b000000: begin // r-type

        case(func)
            6'b100000: begin // add func

                wreg = 1;
                m2reg = 0;
                wmem = 0;
                aluimm = 0;
                regrt = 0;
                aluc = 4'b0010;
            end

            6'b100010: begin // sub

                wreg = 1;
                m2reg = 0;
                wmem = 0;
                aluimm = 0;
                regrt = 0;

```

```

        aluc = 4'b0110;
    end

    6'b100101: begin // or
        wreg = 1;
        m2reg = 0;
        wmem = 0;
        aluimm = 0;
        regrt = 0;
        aluc = 4'b0001;
    end

    6'b100110: begin // xor func
        wreg = 1;
        m2reg = 0;
        wmem = 0;
        aluimm = 0;
        regrt = 0;
        aluc = 4'b1001;
    end

    6'b100100: begin // and func
        wreg = 1;
        m2reg = 0;
        wmem = 0;
        aluimm = 0;
        regrt = 0;
        aluc = 4'b0000;
    end

endcase

end

    6'b100011: begin // l-type and lw
        wreg = 1; // write register
        m2reg = 1; // memory to register
        wmem = 0; // write memory
        aluimm = 1; // alu immediate - means we want to use sign extended immediate over value of qb in alu, if we want to use qb, aluimm should be 0
        regrt = 1;
        aluc = 4'b0010; // add offset ;)
    end

```

```

        end

    endcase

end

endmodule

module muxRegrt (
    input [4:0]rt, // bits (20:16) of dinstOut
    input [4:0]rd, // bits 15:11 of dinstOut
    input regrt,
    output reg [4:0]destReg
);

always @(*) begin
    if (regrt == 0) begin
        destReg = rd;
    end else if (regrt == 1) begin
        destReg = rt;
    end
end

endmodule

module regFile (
    input [4:0]rs, // bits [25:21] dinstOut
    input [4:0]rt, // bits [20:16] of dinstOut
    input [4:0]wrn,
    input [31:0]wbData,
    input wwreg,
    input clock,
    output reg [31:0]qa,
    output reg [31:0]qb
);

reg [31:0] registers [0:31];

integer index; // needs to be out of loop or verilog err

```

```
initial begin
```

```
    registers[0] = 32'h00000000;  
    registers[1] = 32'hA00000AA;  
    registers[2] = 32'h10000011;  
    registers[3] = 32'h20000022;  
    registers[4] = 32'h30000033;  
    registers[5] = 32'h40000044;  
    registers[6] = 32'h50000055;  
    registers[7] = 32'h60000066;  
    registers[8] = 32'h70000077;  
    registers[9] = 32'h80000088;  
    registers[10] = 32'h90000099;
```

```
    for (index = 11; index < 32; index = index + 1) begin
```

```
        registers[index] = 32'b00000000000000000000000000000000;
```

```
    end
```

```
end
```

```
always @(negedge clock) begin
```

```
    if (wwreg == 1) begin
```

```
        registers[wrn] = wbData;
```

```
    end
```

```
end
```

```
always @(*) begin
```

```
    qa = registers[rs];
```

```
    qb = registers[rt];
```

```
end
```

```
endmodule
```

```
// imm32 is set to sign extended value of imm
```

```
module immediateExtender (
```

```
    input [15:0]imm,
```

```
    output reg [31:0]imm32
```

```
);
```

```
always @(*) begin
```

```

        imm32 <= { {16{imm[15]}}, imm[15:0]}; // note to self verilog pg 60 rev 1
    end

endmodule

```

```

module idexe_pipelineRegister(
    input wreg,
    input m2reg,
    input wmem,
    input [3:0]aluc,
    input aluimm,
    input [4:0]destReg, // 5 bits
    input [31:0]fqa,
    input [31:0]fqb,
    input [31:0]imm32,
    input clock,
    output reg ewreg,
    output reg em2reg,
    output reg ewmem,
    output reg [3:0]ealuc,
    output reg ealuimm,
    output reg [4:0]ern,
    output reg [31:0]eqa,
    output reg [31:0]eqb,
    output reg [31:0]eimm32
);

always @(posedge clock) begin
    ewreg = wreg;
    em2reg = m2reg;
    ewmem = wmem;
    ealuc = aluc;
    ealuimm = aluimm;
    ern = destReg;
    eqa = fqa;
    eqb = fqb;
    eimm32 = imm32;
end

```

endmodule

// *****


// End Region Lab 3

// *****


Waveforms:



Design Schematics:

 

I/O Planning:

 

Floor Planning:

